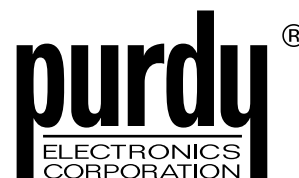


# Optoelectronics

---

## Light Emitting Diodes

### Application Notes



720 Palomar Avenue  
Sunnyvale, CA 94086  
Tel: 408.523.8200 Fax: 408.733.1287  
Email: [email@purdyelectronics.com](mailto:email@purdyelectronics.com)  
[www.purdyelectronics.com](http://www.purdyelectronics.com)

### Drive Methods of LED Lamps

#### DC Drive Techniques

LEDs are current driven devices which means that when using a constant voltage power, a current limiting resistor must be used. Figure 1 shows circuit examples for the DC drive.

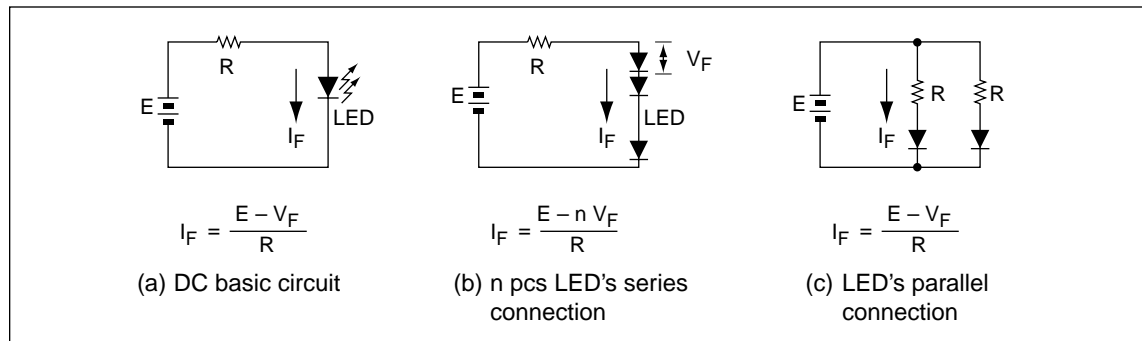


Figure 1

#### AC Drive Techniques

A reverse bias protective circuit is necessary for operating LEDs in an AC mode to prevent exceeding the maximum reverse voltage. Protective diode circuits are shown in Figure 2.

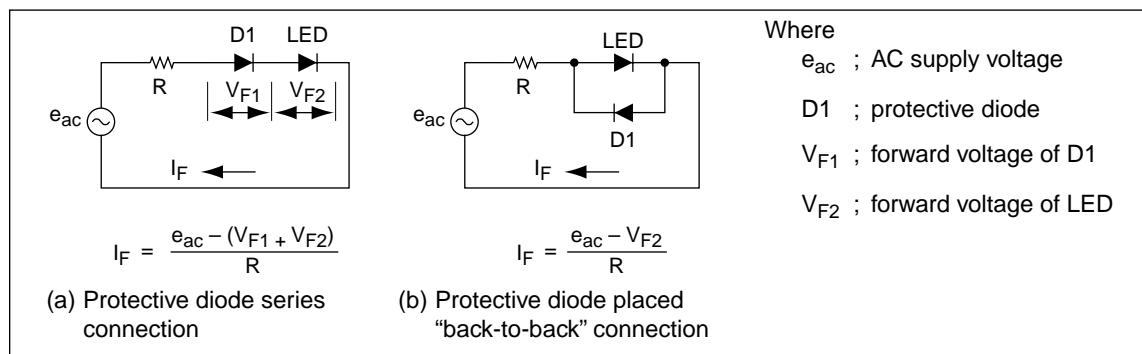


Figure 2

#### Logic Circuit Drive Techniques

Figure 3 illustrates different methods to drive LEDs using integrated circuits.

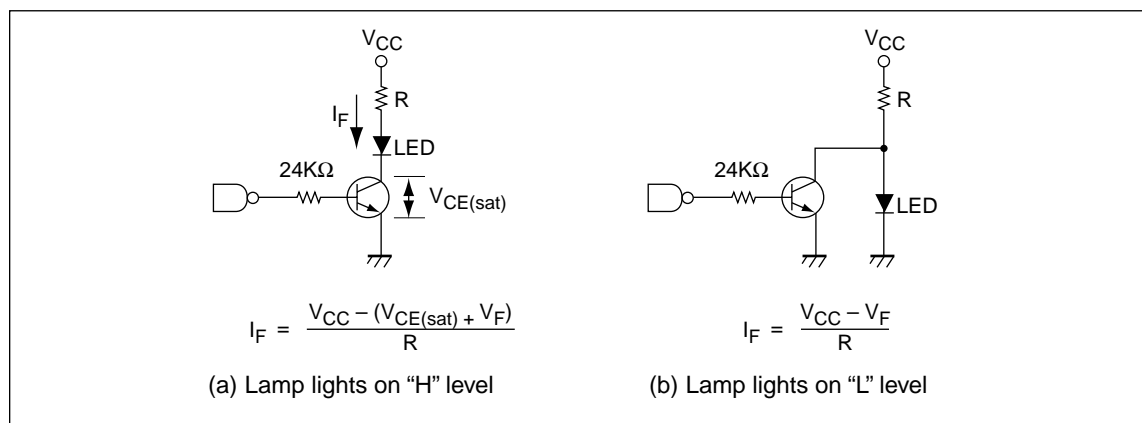


Figure 3

### Allowable Pulse Forward Current of LED Lamps

When a design requires an LED lamp to be operated in the pulse mode, allowable pulse forward current ( $I_{FP}$ ) is determined from the characteristic curves according to driving conditions (pulse width, duty ratio).

#### Applied Pulse

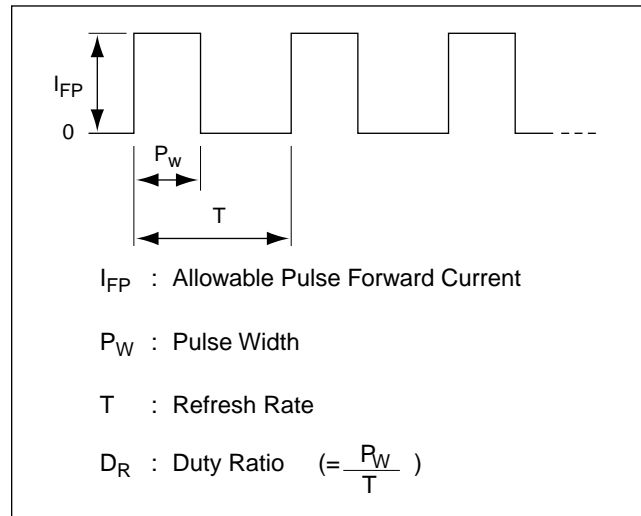


Figure 4

When ambient temperature rises above 25°C,  $I_{FP}$  needs to be determined from Figure 5.

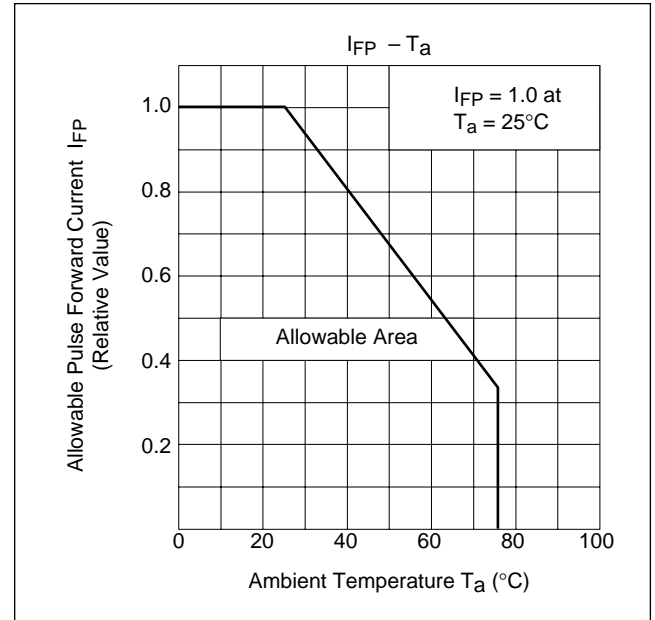


Figure 5

### Characteristic Charts for Determining Allowable Pulse Forward Current

#### GaP Red LEDs

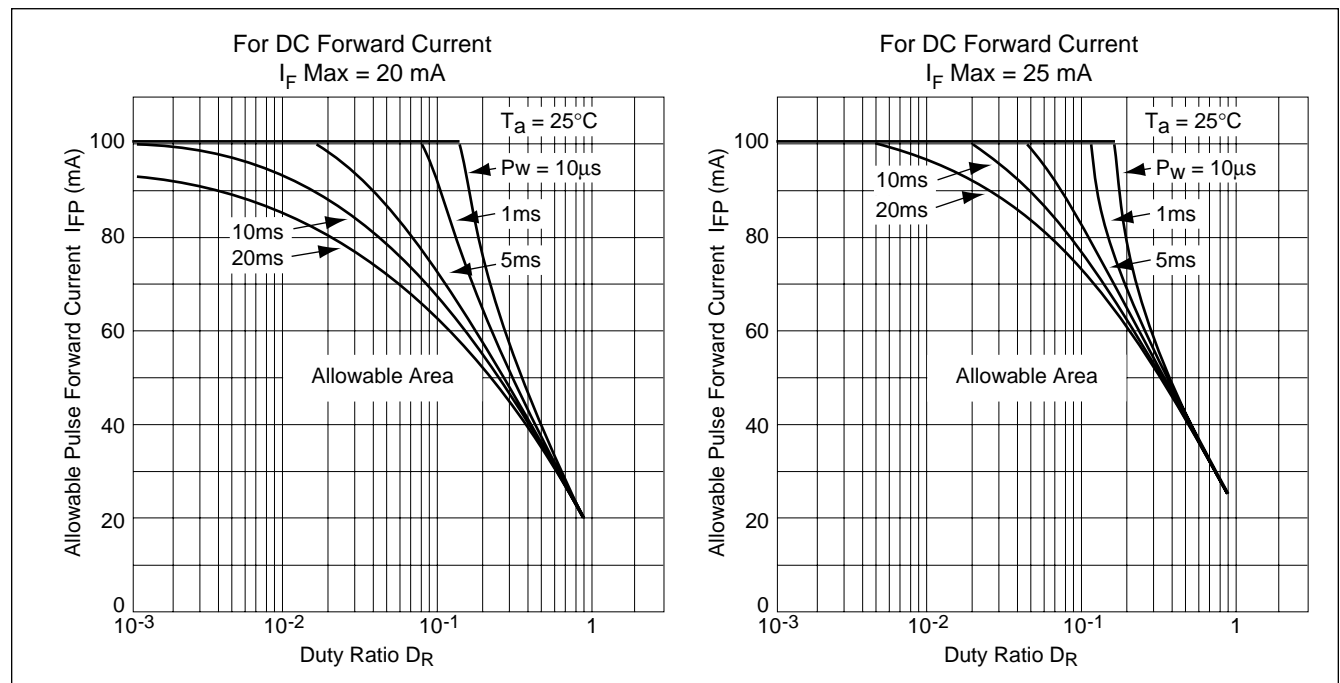


Figure 6

Figure 7

# Application Notes

## Characteristic Charts for Determining Allowable Pulse Forward Current

### GaAsP, GaAlAs, InGaAlP & GaP Green LEDs

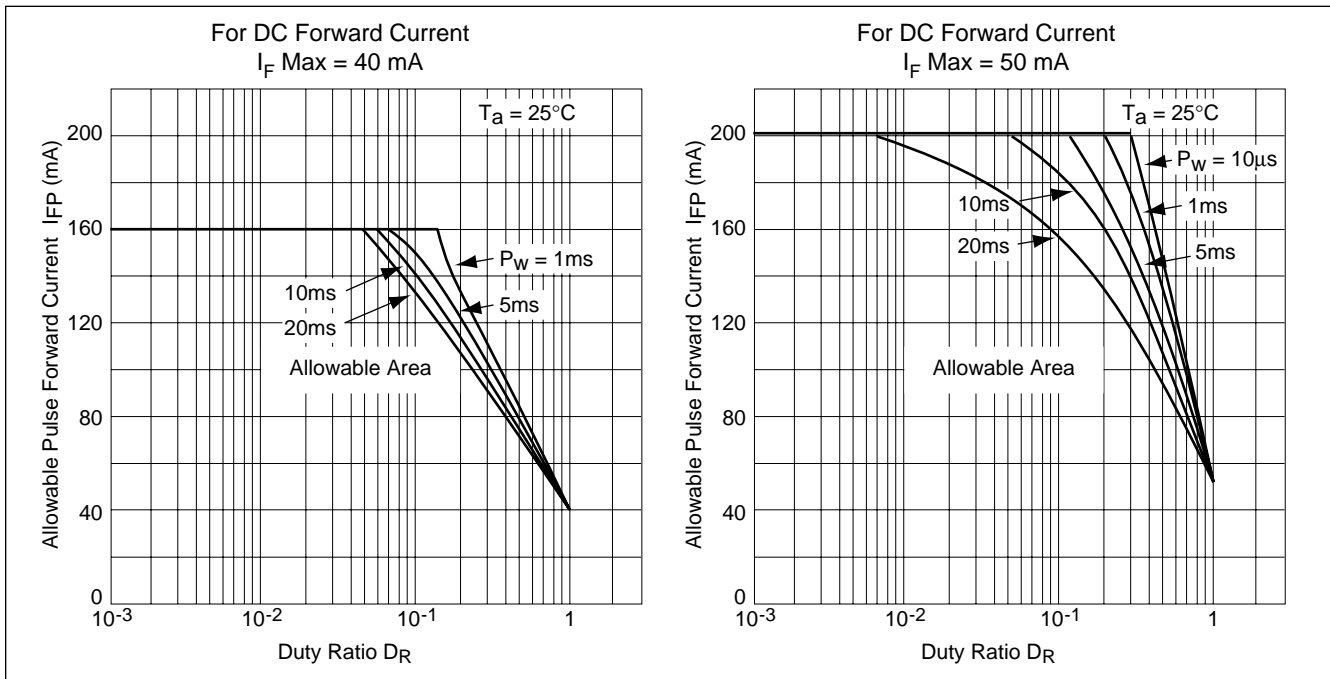


Figure 8

Figure 9

### GaAsP, GaAlAs, InGaAlP & GaP Green LEDs

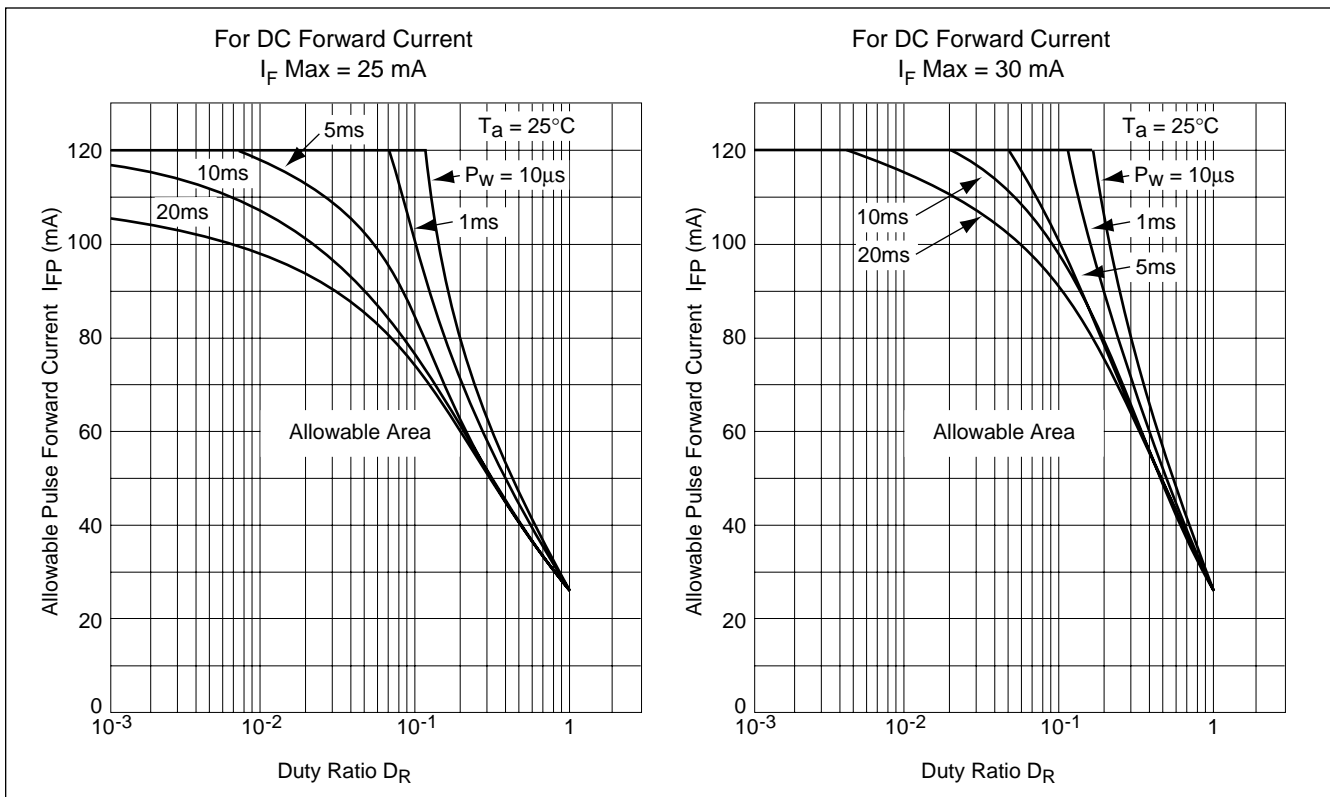


Figure 10

Figure 11